



Reg. 

--	--	--	--	--	--	--	--	--

  
No.:

**G.T.N. ARTS COLLEGE SELF FINANCE  
(AUTONOMOUS)**

(Affiliated to Madurai Kamaraj University || Accredited with 'B' Grade by NAAC)

**END SEMESTER EXAMINATION - NOVEMBER - 2021**

(UNDER OUTCOME BASED EDUCATION (OBE) PATTERN)

**Programme : M.Sc. Physics**


**Course Code : 20PPHC13**


**Course Title : Analog Electronics**

**Date : 16.02.2022**

**Time : 10:00 AM - 1:00 PM**

**Max. Marks : 60**

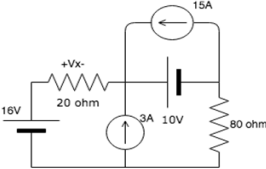Q. No.	SECTION - A (10 * 1 = 10 Marks) Answer ALL Questions	CO(s)	K - Level
1.	Find the value of $V_x$ due to the 16V source.  	CO1	K2
	1.4.2V 2.3.2V 3.2.3V 4.6.3V		
2.	In nodal analysis how many nodes are taken as reference nodes?  1.1 2.2 3.3 4.4	CO1	K2
3.	Most of the electrons in the base of an NPN transistor flow _____.  1.out of the base lead 2.into the emitter 3.into the collector 4.into the base supply	CO2	K1
4.	When the diode is forward bias its depletion region gets _____.  1.larger 2.narrowed 3.positive charge 4.negative charge	CO2	K2
5.	Which of the following properties should an ideal op-amp have _____.  1.infinitely wide bandwidth, infinitely high output impedance and perfect linearity. 2.high DC gain, low input reactance and perfect linearity. 3.infinitely high input impedance, perfect linearity and zero noise. 4.Infinitely high gain, perfect linearity and zero input impedance.	CO3	K1
6.	The given figure represent _____	CO3	K2

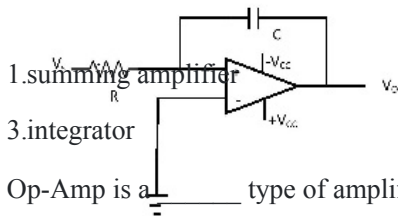

1. summing amplifier  
2. precision rectifier  
3. integrator  
4. differentiator


7. Op-Amp is a \_\_\_\_\_ type of amplifier. CO4 K1  
 1. current  
2. voltage  
3. power  
4. resistance
8. Which type of waveform are output signals in function generator \_\_\_\_\_. CO4 K2  
 1. sine wave  
2. triangular wave  
3. square wave  
4. sine, square and triangular wave
9. How many comparators would a 12-bit flash ADC require? CO5 K2  
 1. 4000  
2. 3095  
3. 4095  
4. 2512
10. Radiation sensor detects radiation level from \_\_\_\_\_ objects. CO5 K2  
 1. electrical  
2. mechanical  
3. radioactive  
4. micro-optics

**Q. No. SECTION - B (5 \* 4 = 20 Marks) CO(s) K - Level**  
**Answer ALL Questions**

11. (a) State the Superposition theorem and list the steps to be followed to solve a network. CO1 K2  
 [OR]  
 (b) State and explain junction diode. CO1 K2
12. (a) Explain the enhancement and depletion mode of MOSFET briefly. CO2 K2  
 [OR]  
 (b) What are the differences between JFET and MOSFET? CO2 K2
13. (a) Explain in detail about inverting amplifier. CO3 K2  
 [OR]  
 (b) Draw the block diagram of operational amplifier and explain it in detail. CO3 K2
14. (a) Describe LC oscillator with neat circuit diagram. CO4 K3  
 [OR]  
 (b) Draw the functional diagram of astable multivibrator. CO4 K3
15. (a) What is a data converter function and explain the different types of data converters. CO5 K3  
 [OR]  
 (b) How does an energy sensor works? CO5 K3


**Q. No. SECTION - C (3 \* 10 = 30 Marks) CO(s) K - Level**  
**Answer any of 3**

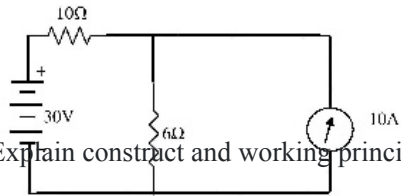16. Find the current through  $6\Omega$  resistor of a network by using superposition theorem. Also find the power through  $6\Omega$  resistor. CO1 K2



17. Explain construct and working principle of BJT in detail. CO2 K3

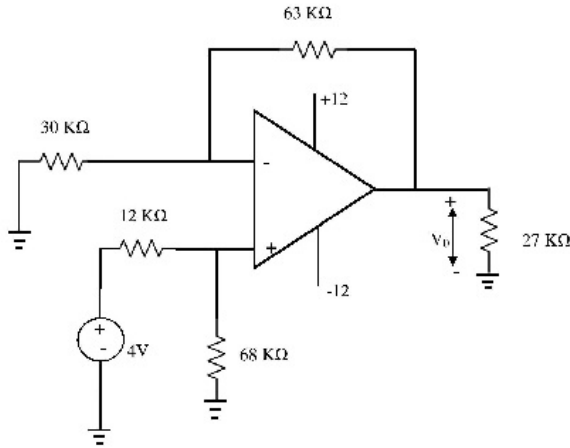18. What do you mean by inverting input and non-inverting input and define input impedance and output impedance by drawing the schematic of op-amp. CO3 K3



19. With neat diagram explain the working of timers. CO4 K4

20. What are the different types of sensors? List it down its classification and their respective application. CO5 K4

\*\*\*\*\*